

- Note : 1) All Questions are compulsory.**  
**2) Figures to right indicate full marks.**

- Q.1. Attempt any three of the following.** 15 M
- Explain digital signal. Also write it's applications.
  - Perform
    - $(653)_8 - (177)_8$
    - $(72)_{16} \times (39)_{16}$
  - Write a short note on Error Correcting Codes.
  - Perform the following binary operation.
    - $(101.11)_2 \times (111.01)_2$
    - $(110\ 110)_2 \div (101)_2$
  - Subtract using 2's complement  $(11011011)_2$  from  $(0101010)_2$
  - Explain Gray code with it's advantages.
- Q.2. Attempt any three of the following:** 15
- Explain basic gates with it's symbol and truth table.
  - Write a short notes on OR gate and AND gate.
  - Prove the following using Boolean laws.
    - $(AB + C) \cdot (AB + D) = AB + CD$
    - $(x + xy)(x + \bar{y})(x + z) = x$
  - Simplify using k-map and realize it using minimum number of gates.  
 $y = \sum m(1, 3, 7, 11, 15) + d(0, 2, 5)$
  - Explain NAND gate and NOR gate with it's symbol and truth table.
  - State and prove De-Morgan's theorem and realize it using basic gates.
- Q.3. Attempt any three of the following** 15
- Describe half subtractor with help of circuit diagram and truth table.
  - Write a short note on fast multiplier.
  - What is comparator circuit? Also explain it's working.
  - Draw circuit and explain working of XS-3 adder.
  - Design BCD to 7 segment decoder. Realize the circuit using NAND gates only.
  - Explain and implement Binary to Gray Code convertor circuit.
- Q.4. Attempt any three of the following.** 15
- Explain clocked S-R flip - flop using four NAND gates.
  - Discuss different applications of flip-flops.
  - Explain with diagram the working of 1 : 8 demultiplexer.
  - Write a short note on Multiplexer.
  - Implement full adder circuit using 4 :1 mux.
  - How S-R flip flop can be used to work as T flip-flop? Explain it.
- Q.5. Attempt any three of the following.** 15
- Write the difference between serial shifting and parallel shifting of data in shift register.
  - Design a synchronous decade counter using D flip-flop.
  - Write a short note on buffer register.
  - Explain working of ripple counter.
  - Write a short note on Johnson Counter.
  - Write truth table for mod 6 counter in IC 7492.