

DLA

DURATION: - 2½ hrs

712021223

MARKS:- 75

Note: - (1) All questions are compulsory.

(2) All questions carry equal marks.

(3) Figures to the right indicates full marks

Q.1 Attempt Any 3

15M

- a) Draw Truth-table of basic gates with its symbol and logical Expression
- b) Write the rule of binary addition, binary multiplication, and subtraction
- c) Convert the following number system
- i) $(105)_{10} = (\underline{\hspace{2cm}})_2$
- ii) $(11011)_2 = (\underline{\hspace{1cm}})_{10}$
- d) Draw block diagram of fulladder, with its Truth-table and logical implementation
- e) Explain two bit comparator with Truth-table
- f) Explain 3:8 decoder with Truth-table

CO1-U

CO1-U

CO1-U

CO2-R

CO2-R

CO2-R

Q.2 Attempt Any 3

15M

- a) Solve using k map $y = \sum m (0,1,3,5)$
- b) What is universal Gate, why it is called so
- c) Implement basic gate using NOR gate
- d) Design 1:8 Demultiplexor with its Truth-table and implementation
- e) Design and implement Binary to Gray code convertor
- f) Compare combinational and sequential logic circuit

CO1-R

CO2-U

CO2-R

CO2-R

CO4-R

CO3-R

Q.3) Attempt Any 3

15M

- a) Explain SISO shift register
- b) Explain with block diagram J-K flip-flop
- c) Write the Expression in standard SOP form;
 $y = \bar{A}BC + AB + AC + \bar{A}\bar{C} + \bar{A}B$
- d) Write the logical expression in canonical form for the Truth-table given below:

CO4-U

CO4-U

CO3-U

CO3-U

A	B	C	y
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

e) Implement following expression using basic gate

i) $y = \bar{A}BC + \bar{A}B\bar{C} + ABC + A\bar{B}C$

ii) $y = A\bar{B} + ABC + \bar{A}\bar{B}\bar{C} + ACD$

f) Write a short notes on Binary Anathematic and logic unit

CO2-U

CO5-U

15M

Q.4) Attempt Any 3

a) Data bits 1011 have to be transmitted. Construct the odd parity 7 bit hamming code for given data

b) Explain multiplexer with its type

c) Explain binary multiplication and division Algorithm

d) State and proof Demorgan's theorem

e) Design 4 bit ripple counter

f) Design 3 bit Asynchronous up counter

CO1-U

CO3-U

CO5-U

CO2-R

CO3-R

15M

Q.5) Attempt Any 3

a) Draw and explain the block diagram of combination of circuit, Enlist example

b) Proof the following using basic boolean's law

i) $A + AB = A$ ii) $A + \bar{A}B = A + B$

c) Compare Encoder and Decoder

d) Write a short notes on: "Error Detection & Error Correction"

e) Draw block diagram of 4:1mux with Truth-table and logical implementation

f) Enlist "Boolean laws"

CO2-R

CO1-R

CO4-U

CO2-U

CO3-R

CO1-U