

Duration: 2.30 Hours

H19NDSA

Marks:- 75

- Note:- 1) All questions are compulsory  
 2) All questions carry equal marks  
 3) Figures to the right indicate maximum marks.

**Q.1 Attempt any four of the following: ( any 4 )**

(20 M)

- 1) Explain and mention the universal gates.
- 2) Explain the NAND gate. Draw its symbol and write its truth table.
- 3) What are the major functions of an IO module ?.
- 4) Design 3 bit synchronous counter using SR flip flops.
- 5) Explain data transfer techniques of DMA.
- 6) List the various performance measure metrics of computer.

**Q.2) Attempt any four of the following: ( any 4 )**

(20 M)

- 1) Design a 3bit synchronous counter using JK flip flops.
- 2) Give different instruction formats.
- 3) Explain and mention the universal gates.
- 4) Explain memory hierarchy.
- 5) With the help of circuit diagram explain the full adder.
- 6) Explain JK flip flop.

**Q.3) Attempt any four of the following: ( any 4 )**

(20 M)

- 1) Explain with example two way set associative mapping technique.
- 2) Write short note on : RISC & CISC processors.
- 3) Explain different allocation policies.
- 4) Differentiate between SRAM & DRAM.
- 5) Write short note on Interrupt driven IO.
- 6) Explain IO addressing & its modes.

**Q.4) Attempt any three of the following**

(15 M)

- 1) Minimize the following expression using the K-map.

$$Y = \sum m(1,5,6,7,11,12,13,15)$$

- 2) Write short note on polling
- 3) Explain multiple –Bus hierarchies
- 4) Simplify the function using K-map draw simplified circuit diagram  
 $F(A,B,C,D) = (A+B+C+\bar{D}) (A+B+\bar{C}+\bar{D}) (\bar{A}+\bar{B}+\bar{C}+\bar{D}) (\bar{A}+\bar{B}+C+D)$
- 5) Write comparison between computer architecture and computer organization
- 6) Simplify the expression given below using K-map & draw simplified circuit

$$Y = \sum m(1,3,7,11,15) + d(0,2,5)$$

XXXXXXXXXXXX